

Finite State Machines

CS 64: Computer Organization and Design Logic

Lecture #16

Winter 2020

Ziad Matni, Ph.D.

Dept. of Computer Science, UCSB

Administrative

- Lab 8 due tomorrow
- Final Exam Announcements
 - Will be 2 hours long – not 3 hours
 - From 7:30 PM – 9:30 PM
 - Practice Exam is on our website
- I will have office hours on Friday from 1 – 2 pm

What's on the Final Exam?

What's on It?

- Everything we've done this quarter, incl. this week's lectures

What Should I Bring?

- Your pencil(s), eraser, MIPS Reference Card (printed on **1 page**)
- THAT'S ALL!

What Else Should I Know/Do?

- **The exam is 2 hours long!** (DSP time will match accordingly)
- **IMPORTANT**: Come to the classroom 5-10 minutes EARLY
- **If you are late, I may not let you take the exam**
- **IMPORTANT**: Use the bathroom before the exam – once inside, you cannot leave
- I will have some of you re-seated
- Bring your UCSB ID

Lecture Outline

- Finite State Machines
 - Moore vs. Mealy types
 - State Diagrams
 - Figuring out a circuit for a FSM

If a combinational logic circuit is an implementation of a ***Boolean function***,


then a sequential logic circuit can be considered an implementation of a ***finite state machine***.

Finite State Machines (FSM)

- A **State** = An output or collection of outputs of a digital “machine”
- A **Machine** = A computational entity that predictably works based on one or more input conditions and yields a logical output
- A Finite State Machine: An **abstract machine** that can be in **exactly one of a finite number of states at any given time**


Finite State Machines (FSM)

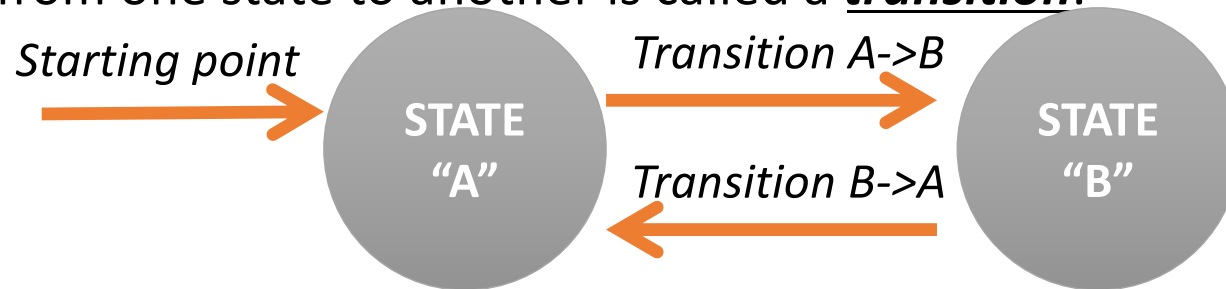- The FSM can change from one state to another in **response to some external inputs**
- The change from one state to another is called a **transition**.



- An FSM is defined by **a list of its states**, its **initial state**, and **the conditions for each transition**.

Example of a Simple FSM: The Turnstile

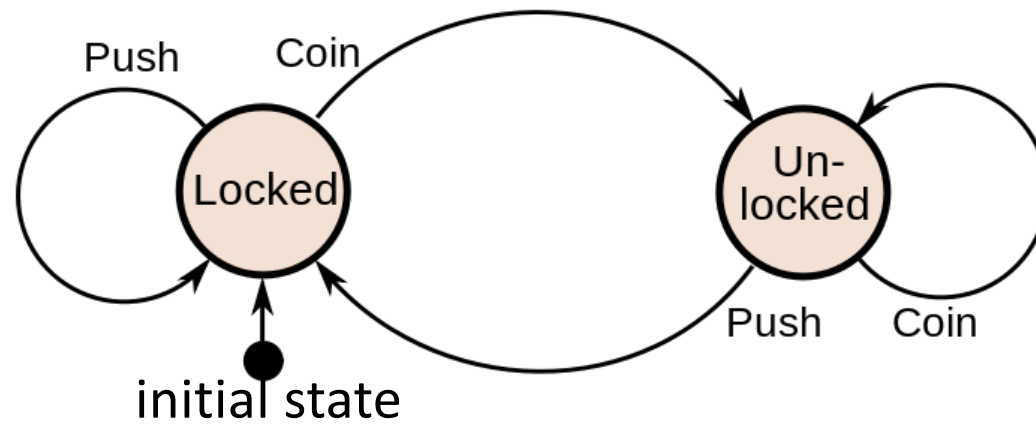


State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.

Example of a Simple FSM: The Turnstile


This is called a
state diagram

 

State Transition Table

Current State	Input	Next State	Output
Locked	Coin	Unlocked	Unlocks the turnstile so that the customer can push through.
Locked	Push	Locked	Nothing – you’re locked! 😊
Unlocked	Coin	Unlocked	Nothing – you just wasted a coin! 😊
Unlocked	Push	Locked	When the customer has pushed through, locks the turnstile.

General Form of FSMs

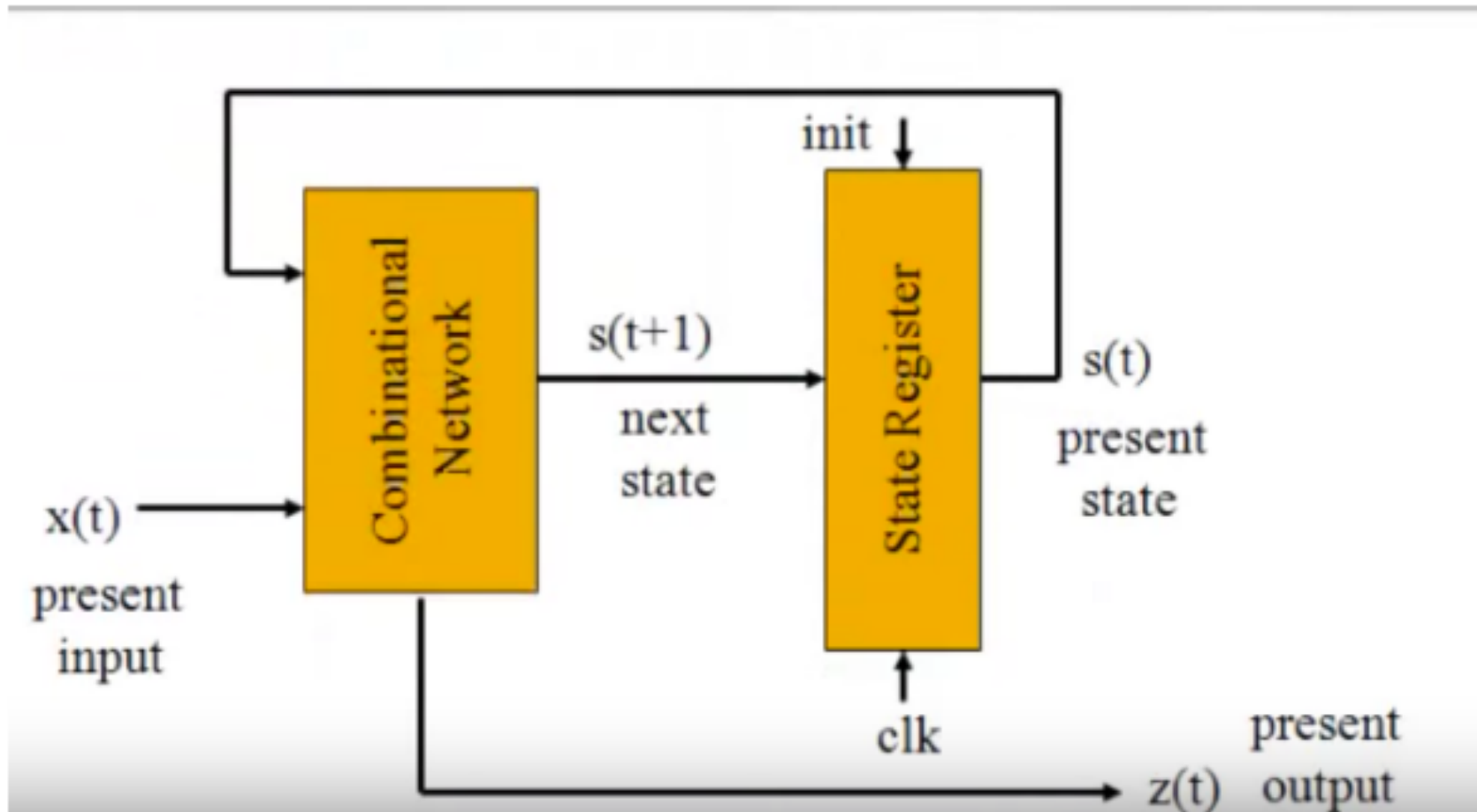

FSM Types

There are 2 types/models of FSMs:

- **Moore machine**


- Output is function of present state only

- **Mealy machine**

- Output is function of present state *and* present input


Moore Machine

Output is function of present state only

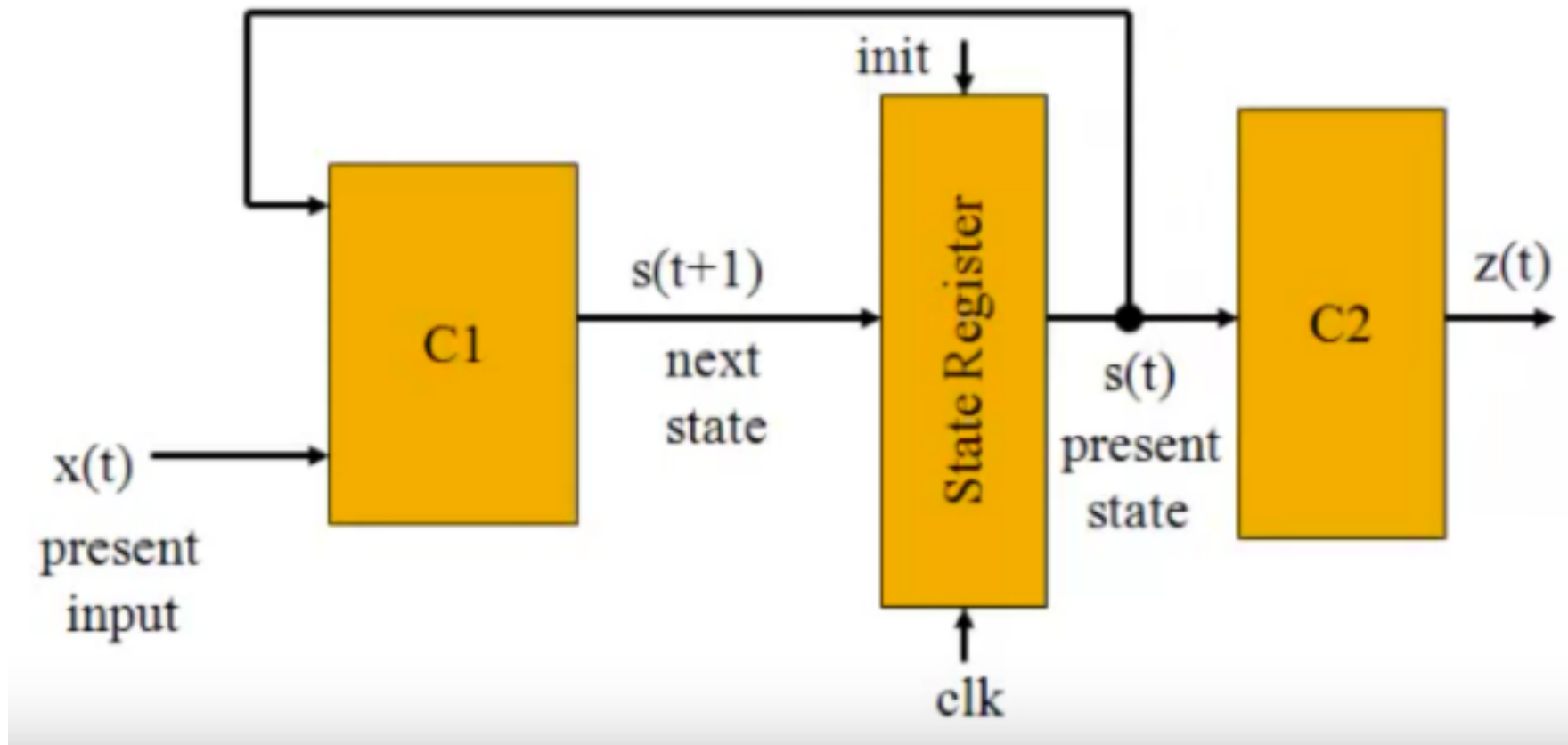

Represented
by Q

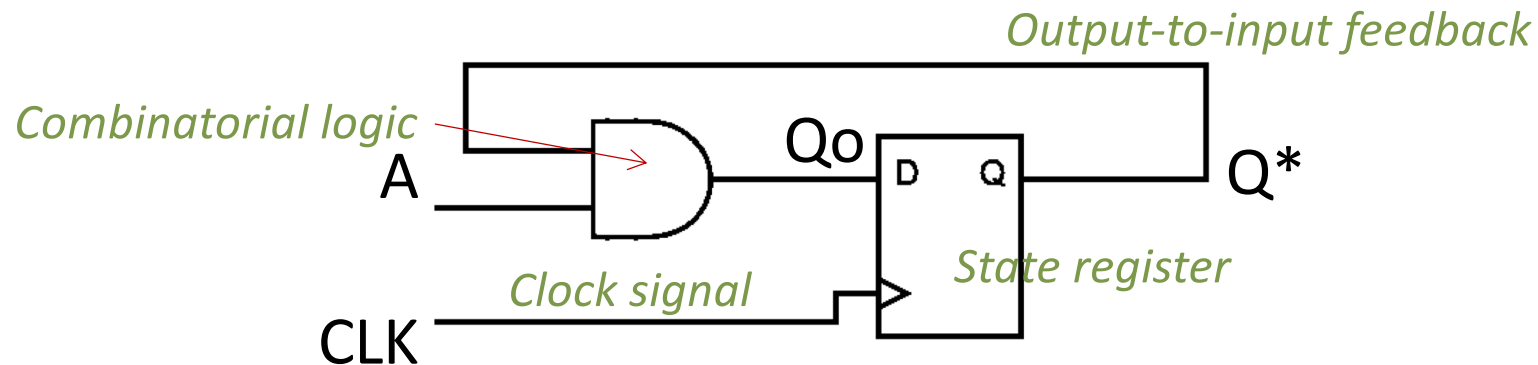Example of a Moore Machine (*with 1 state*)



$$Q^* = Q_0 \cdot A$$


(read as: the next-state of Q will be $Q_0 \cdot A$)

i.e. ***On the next rising edge of the clock***, the output state – aka the output of D-FF (Q^*) – will become the previous value of Q (Q_0) **AND** the value of input A

Example of a Moore Machine (with 2 states + 1 output)

Represented by
Q0 and Q1 (states)
and Z (output)

Output is function of present state only

 


On the next rising edge of the clock, the output state Q0 will be $Q0.A$ and the output state Q1 will be ... (not shown here, but you get the idea)
Also, the circuit output Z will become $Q0 + Q1$

NOTE: CLK is NOWHERE IN THE EQUATION!!!


Mealy Machine

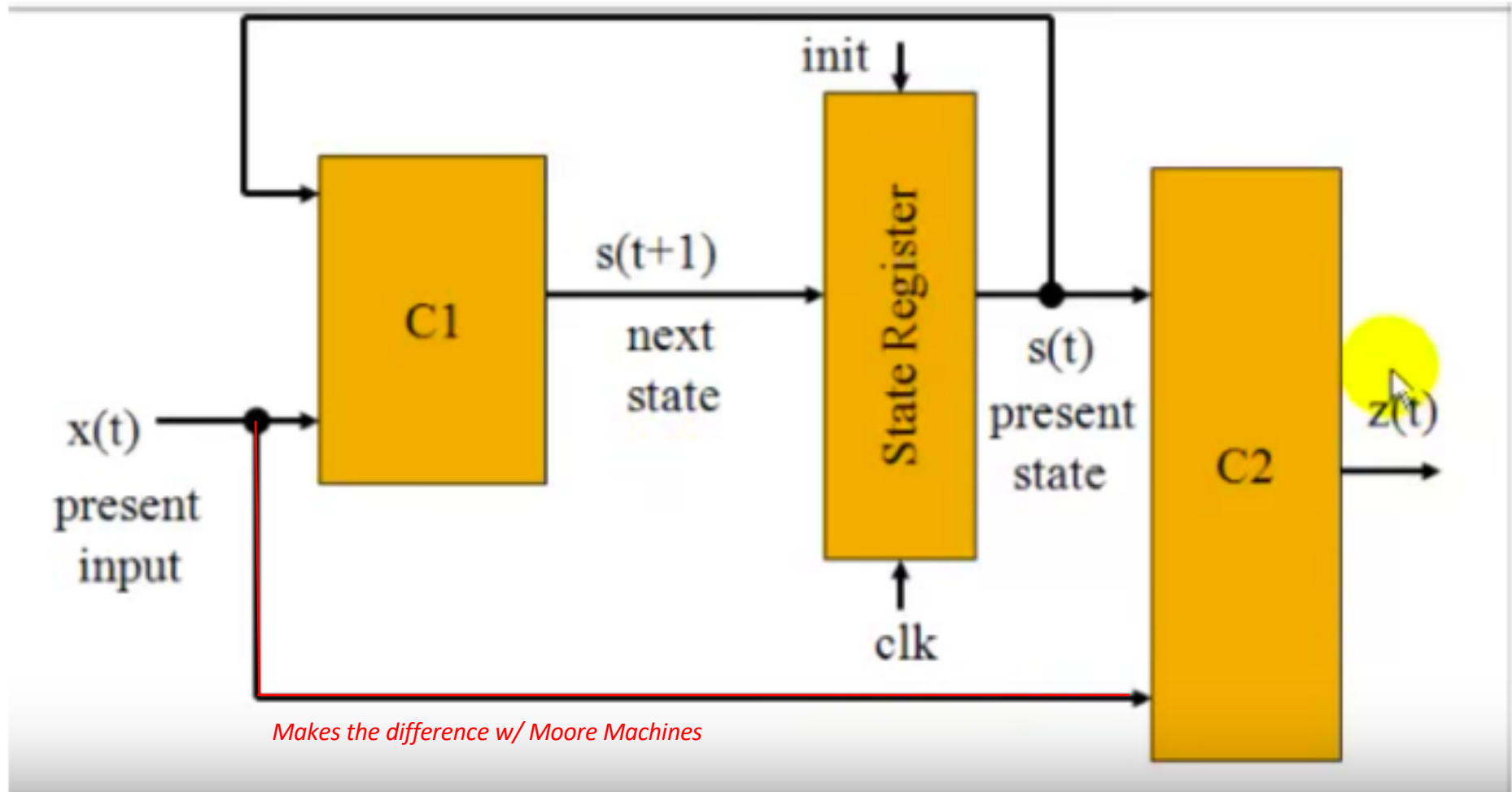Output is function of present state and present input



 Example of a Mealy Machine

Output is function of present state **and** present input



$$Z = (Q^* + A + B) = (Q_0 \text{ XOR } A) + (A + B)$$

On the next rising edge of the clock, the output of the entire circuit (Z) will become ...etc...

Example of a Moore FSM

WASHER_DRYER

- Let's “build” a sequential logic FSM that acts as a controller to a *simplistic* washer/dryer machine
- This machine takes in various inputs in its operation (we'll only focus on the following sensor-based ones):

Coin is in (vs it isn't in)

Soap is present (vs it's used up)

Clothes are still wet (vs clothes are dry)

- This machine also issues 1 output while running:

“Done” indicator

Machine Design

- We want this machine to have **4 distinct states** that we go from one to the next in this sequence:

1. Initial State

- Where we are when we are waiting to start the wash

2. Wash


- Where we wash with soap and water

3. Dry


- Where we dry the clothes

4. Done

State Diagram for Washer-Dryer Machine

 
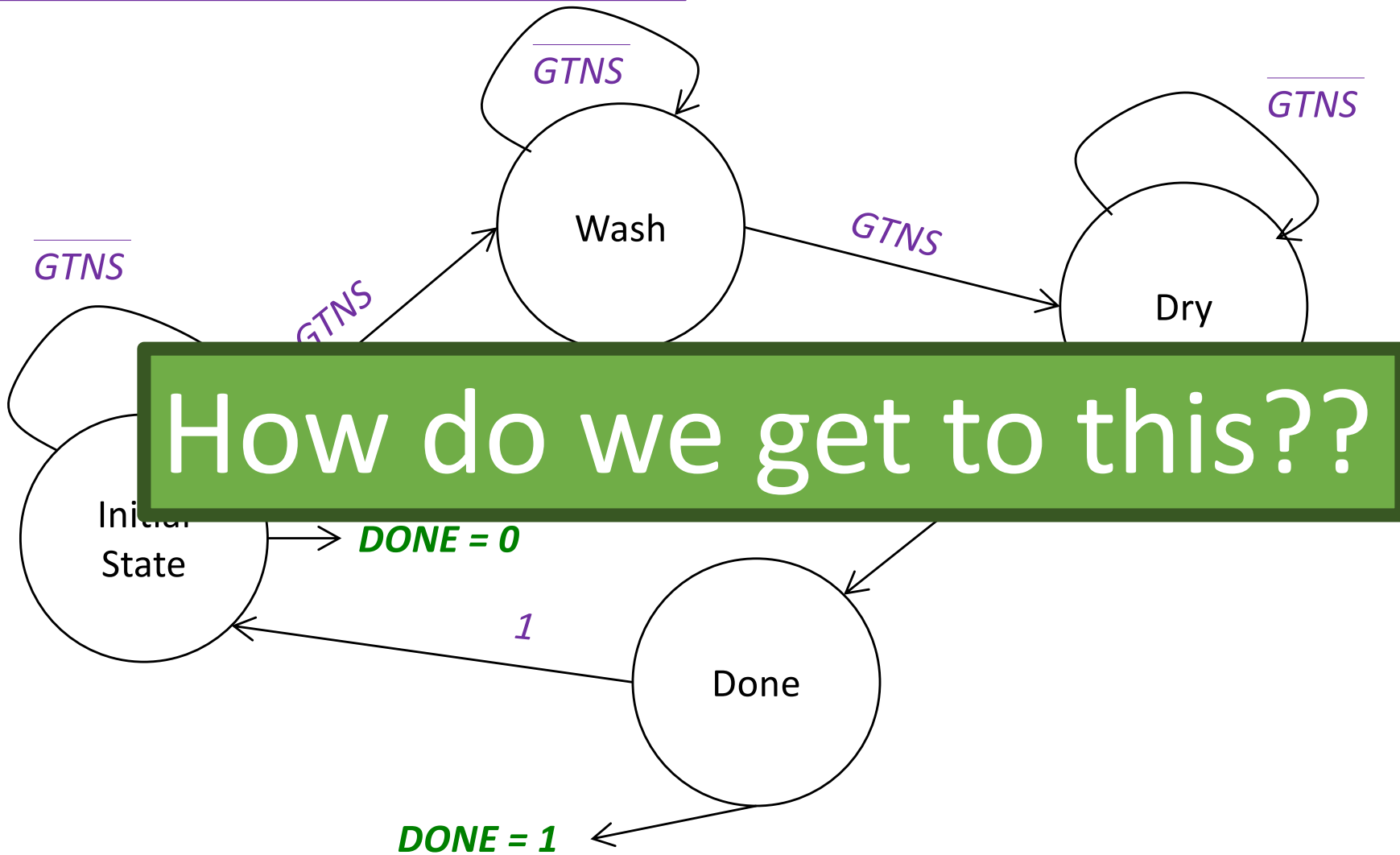
$$GTNS = \overline{COIN_IN} + \overline{NO_SOAP} + \overline{CLTHS_DRY}$$



Combining the Inputs

Coin is in (vs it isn't in)

Soap is no longer detected (vs it's still there)

Clothes are now dry (vs clothes are still wet)

- Let's create a variable called **GTNS** (i.e. Go To Next State)
- GTNS is 1 if **any** of the following is true:
 - Coin is in
 - Soap is no longer detected
 - Clothes are now dry
 - **I assume that these 3 inputs to be mutually exclusive**

What's Going to Happen?

1/2

Coin is in (vs it isn't in)

Soap is no longer detected (vs it's still there)

Clothes are now dry (vs clothes are still wet)

- We start at an “**Initial**” state whenever we start up the machine
 - Let's assume this stage is when you'd put in the soap and clothes
 - Once input “**Coin is in**” is 1, **GTNS** is now 1
 - This event triggers leaving the current state to go to the next state
- This is followed by the next state, “**Wash**”
 - “**Coin inserted**” is now 0 at this point (so **GTNS** goes back to 0)
 - While soap is still present, **GTNS** goes back to 0
 - When the input “**Soap is no longer present**” goes to 1, **GTNS** goes to 1
 - This event triggers leaving the current state to go to the next state

What's Going to Happen?

2/2

Coin is in (vs it isn't in)



Soap is no longer detected (vs it's still there)

Clothes are now dry (vs clothes are still wet)

- This is followed by the next state, “**Dry**”
 - This new state sets an output that triggers a timer
 - The input “**Soap is no longer present**” goes to 0, so **GTNS** is 0 also
 - While the input “**Clothes are now dry**” is 0 , **GTNS** remains at 0 too
 - When the input “**Clothes are now dry**” is 1, **GTNS** changes to 1
 - This event triggers leaving the current state to go to the next state
- This is followed by the next and last state, “**Done**”
 - When you're here, you go back to the “initial” state
 - No inputs to consider: you do move this regardless


State Diagram for Washer-Dryer Machine

$$GTNS = COIN_IN + NO_SOAP + CLTHS_DRY$$

  


Unconditional Transitions

 - Sometimes the transition is unconditional
 - Does not depend on any input –
you go from **State X** to **State Y** regardless...
- We then diagram this as a “**1**” (for “always does this”)



Representing The States

 

- How many bits do I need to represent all the states in this Washer-Dryer Machine?
- There are 4 unique states (including “init”)
 - So, 2 bits
- If my state machine will be built using a memory circuit (most likely, a D-FF), how many of these should I have?
 - 2 bits = 2 D-FFs
- There is another scheme to do this called “One Hot Method”
 - Will be explained later...

State	S1	S0
Initial	0	0
Wash	0	1
Rinse	1	0
Dry	1	1

Example of a Moore FSM 2

DETECT_1101


- Let's build a sequential logic FSM that **always detects a specific serial sequence of bits: *1101***
- We'll start at an "Initial" state (S0)
- We'll first look for a **1**. We'll call that "State 1" (S1)
 - Don't go to S1 if all we find is a **0**!
- We'll then keep looking for another **1**. We'll call that "State 11" (S2)

Example of a Moore Machine 2


DETECT_1101

- Then... a **0**. We'll call that "State 110" (S3)
- Then another **1**.
We'll call that "State 1101"(S4) – this will also output a **FOUND** signal
- We will always be detecting "1101" (it doesn't end)
So, as SOON as S4 is done, we keep looking for 1s or 0s
- Example: if the input stream is **111101110101101000011111011011**
we detect "1101" at ↑ ↑ ↑ ↑ ↑

State Diagram 2

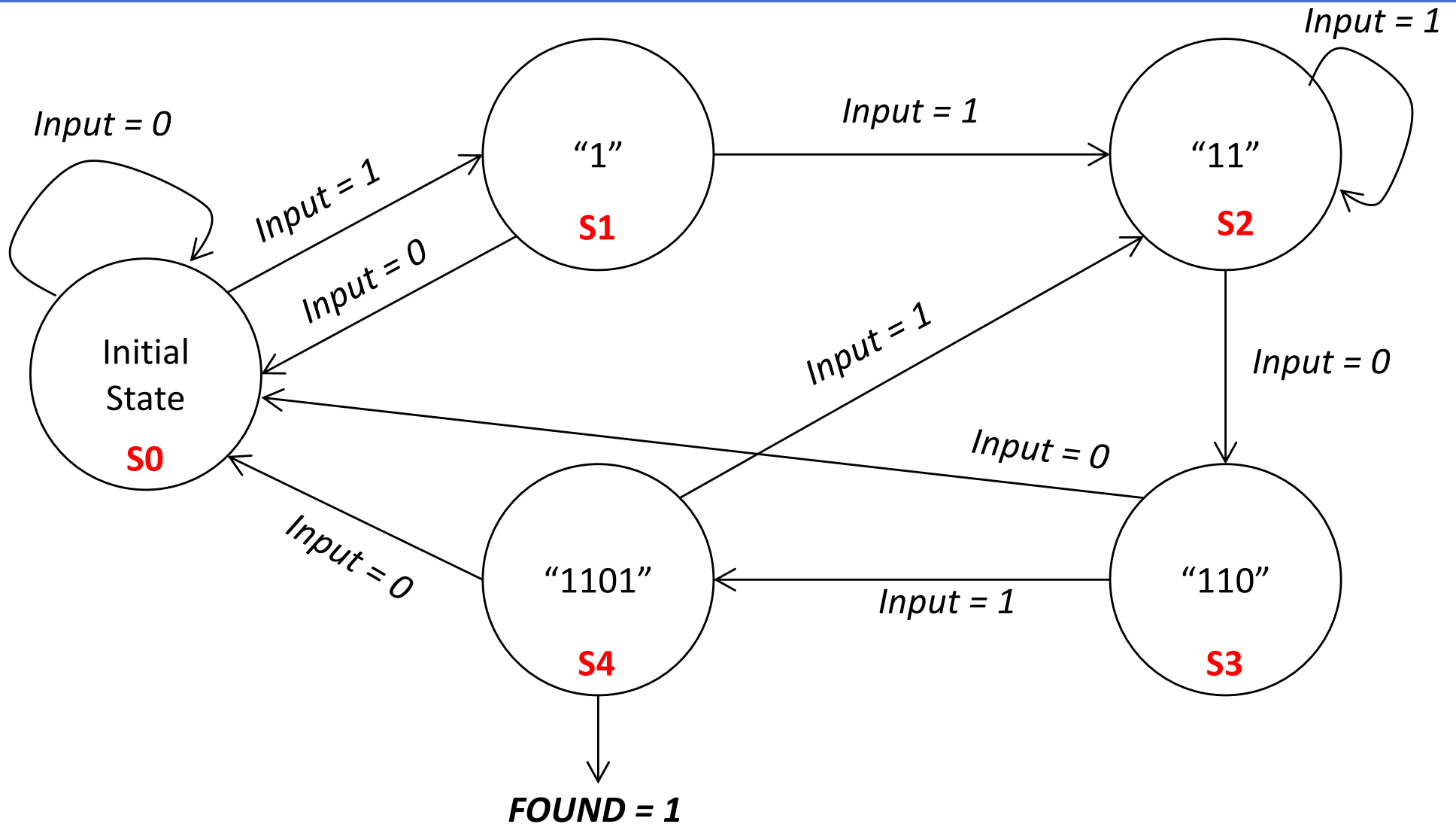

Representing The States

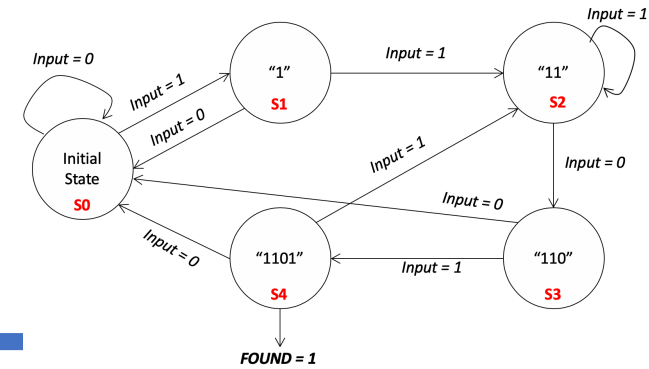

- How many bits do I need to represent all the states in this “Detect 1101” Machine?
 - So, 3 bits
- There are 5 unique states (including “init”)
 - So, 3 bits
- How many D-FFs should I have to build this machine?
 - 3 bits = 3 D-FFs

State	B2	B1	B0
Initial	0	0	0
Found “1”	0	0	1
Found “11”	0	1	0
Found “110”	0	1	1
Found “1101”	1	0	0
N/A	1	0	1
	1	1	X

Designing the Circuit for the FSM

1. We start with a T.T

- Also called a “State Transition Table”

2. Make K-Maps and simplify

- Usually give your answer as a “sum-of-products” form

3. Design the circuit

- Have to use D-FFs to represent the state bits



Note: We are ignoring the N/A states

1. The Truth Table (The State Transition Table)

State	CURRENT STATE			INPUT(S)	NEXT STATE			OUTPUT(S)
	B2	B1	B0	I	B2*	B1*	B0*	FOUND
Initial	0	0	0	0	0	0	0	0
				1	0	0	1	0
Found "1"	0	0	1	0	0	0	0	0
				1	0	1	0	0
Found "11"	0	1	0	0	0	1	1	0
				1	0	1	0	0
Found "110"	0	1	1	0	0	0	0	0
				1	1	0	0	0
Found "1101"	1	0	0	0	0	0	0	1
				1	0	1	0	1

2. K-Maps for B2* and B1*

State	B2	B1	B0	I	B2*	B1*	B0*	FOUND
Initial	0	0	0	0	0	0	0	0
				1	0	0	1	0
Found "1"	0	0	1	0	0	0	0	0
				1	0	1	0	0
Found "11"	0	1	0	0	0	1	1	0
				1	0	1	0	0
Found "110"	0	1	1	0	0	0	0	0
				1	1	0	0	0
Found "1101"	1	0	0	0	0	0	0	1
				1	0	1	0	1

You need to do this for all state outputs

B2*

B2.B1 B0.I	00	01	11	10
00				
01				
11		1		
10				

- $B2^* = \neg B2 \cdot B1 \cdot B0 \cdot I$

- No further simplification

- $B1^* = \neg B2 \cdot \neg B1 \cdot B0 \cdot I + B2 \cdot \neg B1 \cdot \neg B0 \cdot I + \neg B2 \cdot B1 \cdot \neg B0$

B1*

B2.B1 B0.I	00	01	11	10
00		1		
01		1		1
11	1			
10				

2. K-Map for $B0^*$

Output FOUND

- $B0^* = \neg B2 \cdot \neg B1 \cdot \neg B0 \cdot I$
 $+ \neg B2 \cdot B1 \cdot \neg B0 \cdot \neg I$

$B0^*$

$B2.B1$ $B0.I$	00	01	11	10
00		1		
01	1			
11				
10				

- $FOUND = B2 \cdot \neg B1 \cdot \neg B0$

- Note that FOUND does not need a K-Map. It is always “1” (i.e. True) when we are in state S4 (i.e. when $B2=1, B1=0, B0=0$)

3. Design the Circuit


Note that CLK is the input to ALL the D-FFs' clock inputs. This is a *synchronous machine*.

Note the use of labels (example: B2 or B0-bar) instead of routing wires all over the place!

Note that I issued both B_n and $B_n\text{-bar}$ from all the D-FFs – it makes it easier with the labeling and you won't have to use NOT gates!

Note that the sole output (FOUND) does **not** need a D-FF because it is **NOT A STATE BIT!**

3/9/20

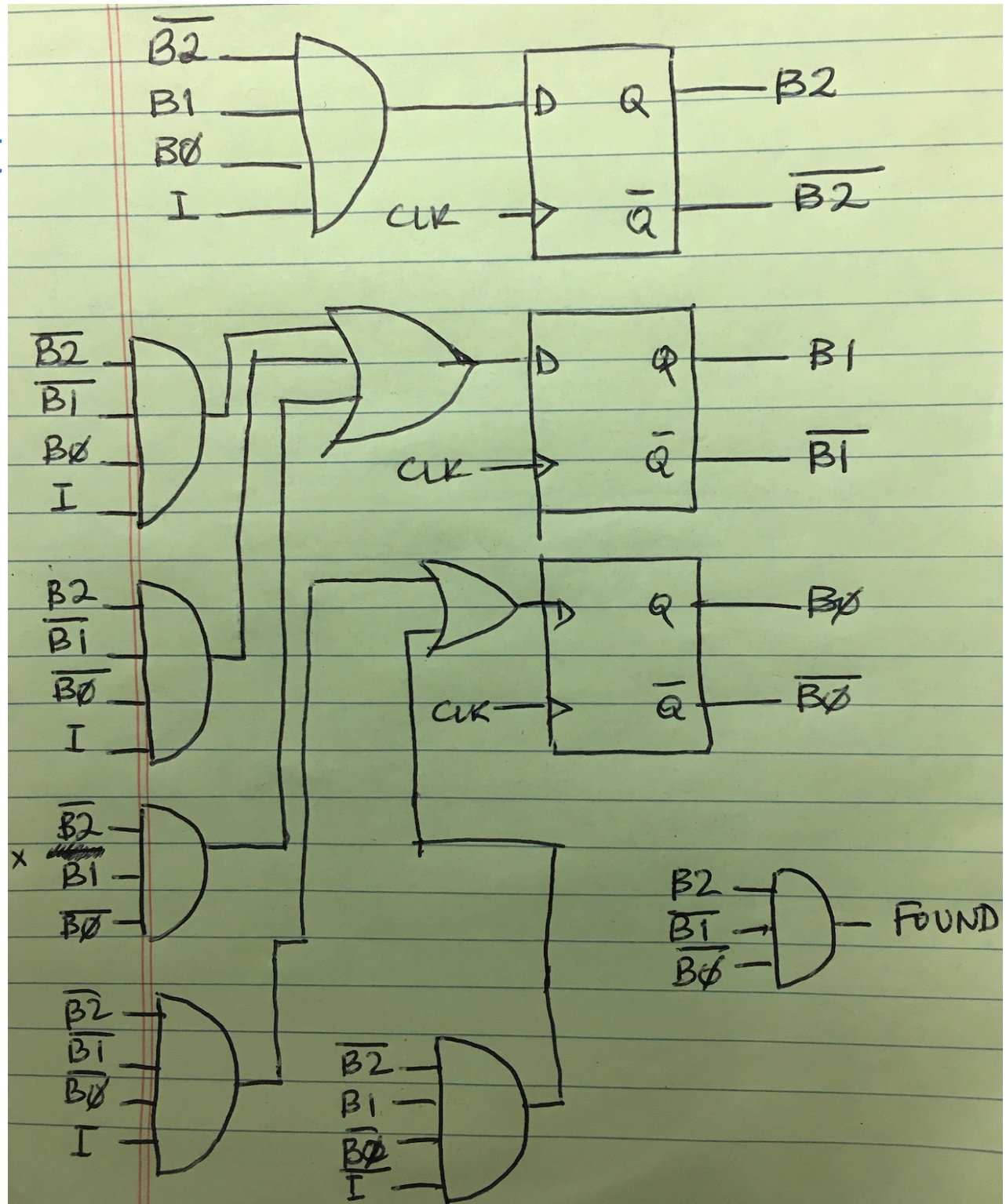

YOUR TO-DOs

- Review this FSM stuff!
- Finish Lab #8!

</LECTURE>